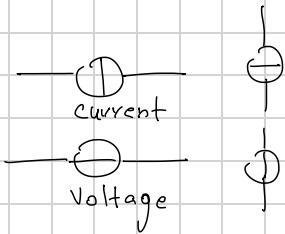




Signals and Systems 2

Adam AlOgaily



$$H(j\omega) = \frac{\text{output}}{\text{excitation input}} \quad \rightarrow \text{complex domain}$$

↓


transfer
Characteristic

Voltage split $\rightarrow \frac{\text{OWN}}{\text{Sum}}$

Current Split $\rightarrow \frac{\text{Other}}{\text{Sum}}$


2025. 9. 10

Example 1: revision

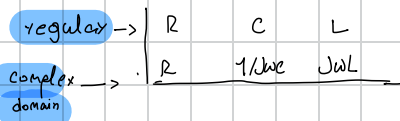

What's the transfer characteristic?

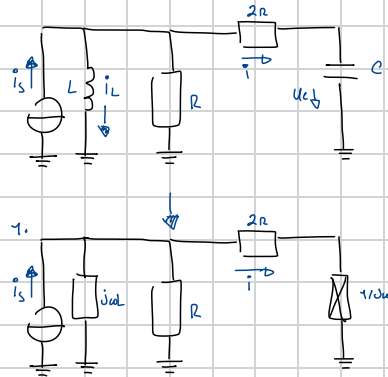1. Assume circuit is in complex domain
2. Current Split
3. Simplify



2. $H(j\omega) = \frac{i}{i_s} = \frac{\text{other}}{\text{sum}} = \frac{R \parallel j\omega L}{R \parallel j\omega L + 2R + 1/j\omega C}$

\rightarrow parallel notation \parallel or \times

$= \frac{\frac{R \cdot j\omega L}{R + j\omega L}}{\frac{R \cdot j\omega L}{R + j\omega L} + 2R + 1/j\omega C} = \frac{R \cdot j\omega L}{R \cdot j\omega L + 2R^2 + 2Rj\omega L + \frac{R + j\omega L}{j\omega C}}$

$= \frac{(j\omega)^2 RLC}{3(j\omega)^2 RLC + 2R^2 j\omega C + R + j\omega L} = \frac{(j\omega)^2 RLC}{3(j\omega)^2 RLC + j\omega(2R^2 C + L) + R}$

$= \frac{(j\omega)^2 / 3}{(j\omega)^2 + j\omega \left(\frac{2R^2 C}{3RLC} + \frac{L}{3RLC} \right) + R / 3RLC}$

$H(j\omega) = \frac{1/3 \cdot (j\omega)^2}{(j\omega)^2 + j\omega \left(\frac{2R}{3L} + \frac{1}{3RC} \right) + \frac{1}{3LC}}$

Example 2: find output


input $\omega_1 = 0$ $\omega_2 = 1$ $\omega_3 = 5$

$u(t) = [10 + 4\cos(t + 15^\circ) + 3\cos(5t - 40^\circ)]$


transfer characteristic $L \rightarrow 4e^{j15}$ $L \rightarrow 3e^{-j40^\circ}$

$H(j\omega) = \frac{3j\omega + 6}{(j\omega)^2 + 4j\omega + 9}$

System

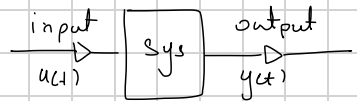

coherent unit system

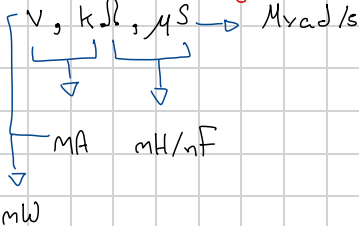

conversion table

ω	\bar{u}	\bar{H}	\bar{y}
0	10	6/9	6.66
1	$4e^{j15}$	3/4	$3e^{j15}$
5	$3e^{-j40}$	$0.6307e^{-j60.4}$	$1.8921e^{-j70.4}$

$H(j\omega)|_{\omega=0} = \frac{6}{9}$

$H(j\omega)|_{\omega=1} = \frac{3j + 6}{(j)^2 + 4j + 9} = \frac{3j + 6}{4j - 1 + 9} = \frac{3j + 6}{4j + 8}$

$\left[\frac{3j + 6}{4j + 8} = \frac{3}{4} \right]$

output (solution)

$y(t) = [6.66 + 3\cos(t + 15^\circ) + 1.8921\cos(5t - 70.4^\circ)] \text{ mA}$

use calc to find $\left[\begin{matrix} \text{substitute} \\ \text{with } \omega \end{matrix} \right]$

2. find complex power \bar{S} of this system

2025. 9. 10

$$H(j\omega) = 0.6307e^{-j60.4}$$

$\omega = 3$

\downarrow
v < 0
form



$$\bar{S} = U I^* = (i)^2 \bar{Z} \rightarrow \text{impedance}$$


$$\bar{S}_0 = (i)^2 Z = (6.66)^2 \cdot 5 = 221.778 \text{ mW}$$

$$\bar{S}_1 = (i)^2 \bar{Z} = (6.66)^2 \cdot (5 + 0.4 \cdot j\omega L) / 2 = 111.243 \text{ mW}$$

$$\bar{S}_2 = (6.66)^2 \cdot (5 + 0.4 \cdot j\omega L) = 110.889 + 44.355j$$

$$i_{rms} = \sqrt{(6.66)^2 + \frac{3^2 + 1.89^2}{2}} = \text{mA}$$

Example 3: Fourier

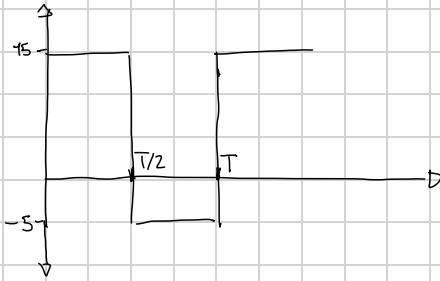

$$\omega_0 = \frac{2\pi}{T} \leftarrow f = \frac{1}{T}$$

$$i = -1 \quad e^{-j\pi} = \cos(\pi) - j\sin(\pi)$$

$$\frac{1}{-j2\pi} \left[15 \left(\frac{e^{-j\pi}}{-1} - 1 \right) - 5 \left(\frac{e^{-j2\pi}}{1} - \frac{e^{-j\pi}}{-1} \right) \right] =$$

$$\frac{1}{-j2\pi} \left[15(-2) - 5(2) \right] = \frac{1}{j2\pi} [-30 - 10]$$

i = 2

$$\frac{1}{-j4\pi} \left[15 \left(\frac{e^{-j2\pi}}{+1} - 1 \right) - 5 \left(\frac{e^{-j4\pi}}{1} - \frac{e^{-j2\pi}}{+1} \right) \right] =$$

iterate for i = 3

$$u(t) = [u_0 + \bar{u}_1 + \bar{u}_2 + \bar{u}_3]$$


$$u_0 = \frac{1}{T} \int_0^T u(t) dt = \frac{1}{T} \left[\int_0^{T/2} 15 dt + \int_{T/2}^T -5 dt \right]$$

$$= \frac{1}{T} \left[15T/2 - (5T - 5T/2) \right] = 5$$

$$\bar{u}_1 = \frac{1}{T} \left[\int_0^{T/2} 15 e^{-j\omega_0 t} dt + \int_{T/2}^T -5 e^{-j\omega_0 t} dt \right]$$


$$= \frac{15 \left(\frac{e^{-j\omega_0 T/2}}{-j\omega_0} - \frac{e^{-j\omega_0 \cdot 0}}{-j\omega_0} \right) - 5 \left(\frac{e^{-j\omega_0 T}}{-j\omega_0} - \frac{e^{-j\omega_0 T/2}}{-j\omega_0} \right)}{-j2\pi i} =$$
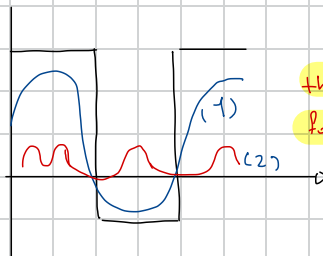
$$\frac{1}{-j2\pi i} \left[15 \left(\frac{e^{-j\pi}}{-1} - 1 \right) - 5 \left(\frac{e^{-j2\pi}}{1} - \frac{e^{-j\pi}}{-1} \right) \right] =$$




third order

fourier expression

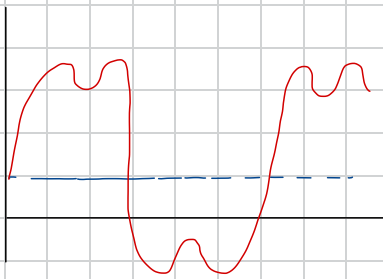

Harmonic
Combination

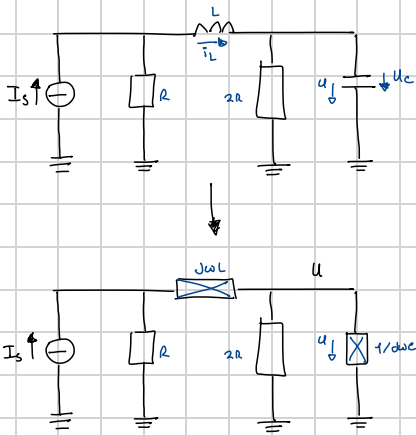Example 4: Find transfer characteristic
of the system





$$\begin{aligned}
 H(j\omega) &= \frac{u}{I_s} = \frac{R}{2R \times 1/j\omega C + R + j\omega L} \cdot \frac{2R}{(2R + 1/j\omega C)} \\
 &= \frac{R}{\frac{2R \cdot 1/j\omega C}{2R + 1/j\omega C} + R + j\omega L} \cdot \frac{2R}{(2R + 1/j\omega C)} \\
 &= \frac{R}{\frac{2R \cdot 1/j\omega C}{2R + 1/j\omega C} + R + j\omega L} \cdot \frac{2R}{(2R + 1/j\omega C)} \\
 &= \frac{2R^2}{\frac{2R \cdot 1/j\omega C}{j\omega C} + \frac{R(2R + 1/j\omega C)}{j\omega C} + \frac{j\omega L(2R + 1/j\omega C)}{j\omega C}} \\
 &= \frac{2R^2}{\frac{2R}{(j\omega C)^2} + \frac{R(2R + 1/j\omega C)}{j\omega C} + \frac{L(2R + 1/j\omega C)}{C}}
 \end{aligned}$$

$\omega)^2 C$

2023.9.11

Fourier transform

time / frequency domains

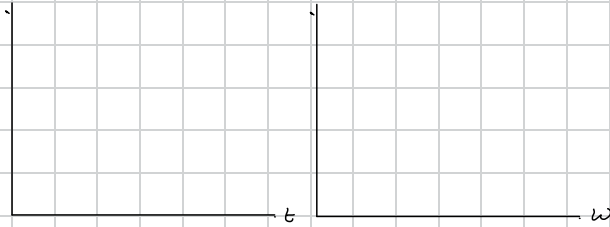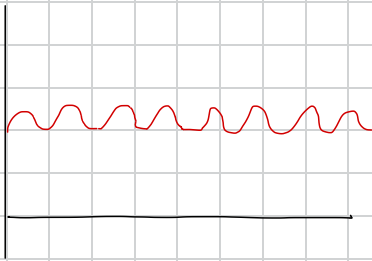

frequencies and their amplitudes

$$F(\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

fourier series and transform can be used for different cases. Series for periodic functions. Transform for any function (integrable)

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(\omega) e^{j\omega t} d\omega$$


Inverse Fourier transform


I. $\mathcal{F}\{x(t)\} = F\{x(t)\}$
 $\mathcal{F}\{x_1(t) + x_2(t)\} = \mathcal{F}\{x_1(t) + x_2(t)\}$

II. $\mathcal{F}\{x(t) e^{-\alpha t}\} = X(j\omega + \alpha)$
 $\alpha > 0!$

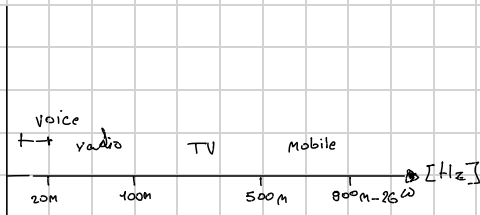III. Modulation theorem

$$\mathcal{F}\{x(t) e^{-j\omega_0 t}\} = X(j(\omega + \omega_0))$$



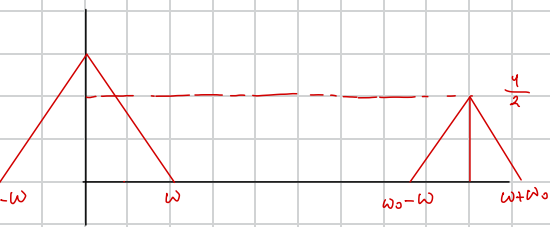

Spectrum of
frequency

$$x(j\omega)$$

$$x(t)e^{-j\omega t}$$

$$x(t)\cos\omega t = x(t) \frac{e^{j\omega t} - e^{-j\omega t}}{2}$$

IV Derivative theory

$$\mathcal{F}\left\{\int_0^t x(\tau) d\tau\right\} = -\frac{x(j\omega)}{j\omega} + \delta(x+\delta)$$

V

