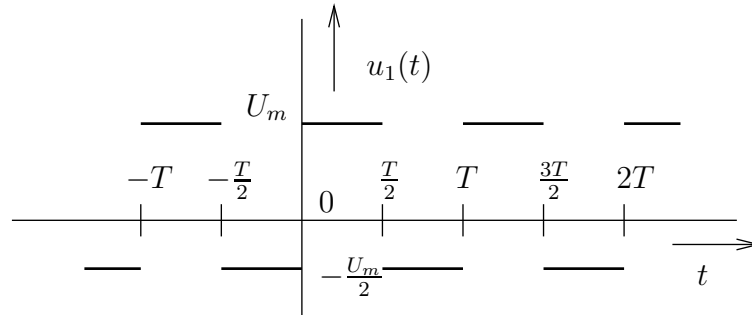


1. The input signal and the response of a system represented by a network are voltages. The frequency response of the system is: $H(j\omega) = \frac{j\omega T}{j\omega T + 2}$ where T is a parameter. The input signal of the system is the periodic voltage signal given in the figure.




- a) Find the three-order Fourier polynomial of the input signal!
- b) Find the response of the system in three-order Fourier polynomial approximation!

Solution

$$\begin{aligned}
 \text{a) } U_p^C &= \frac{1}{T} \int_{t=\langle T \rangle} u_1(t) e^{-jp\omega_0 t} dt, & \langle T \rangle &= \left\{ -\frac{T}{2}; \frac{T}{2} \right\}. \\
 U_0^C &= \frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} u_1(t) dt = \frac{1}{T} \left(\int_{-\frac{T}{2}}^0 \left(-\frac{U_m}{2}\right) dt + \int_0^{\frac{T}{2}} U_m dt \right) = \frac{1}{T} \left(-\frac{U_m T}{4} + \frac{U_m T}{2} \right) = \frac{U_m}{4}, \\
 U_0 &= U_0^C = \frac{U_m}{4}. \\
 \text{For } p > 0: U_p^C &= \frac{1}{T} \left(\int_{-\frac{T}{2}}^0 \left(-\frac{U_m}{2}\right) e^{-jp\frac{2\pi}{T}t} dt + \int_0^{\frac{T}{2}} U_m e^{-jp\frac{2\pi}{T}t} dt \right) = \\
 &= \frac{U_m}{T} \left(-\frac{1}{2} \frac{jT}{2\pi p} \left[e^{-jp\frac{2\pi}{T}t} \right]_{-\frac{T}{2}}^0 + \frac{jT}{2\pi p} \left[e^{-jp\frac{2\pi}{T}t} \right]_0^{\frac{T}{2}} \right) = \frac{jU_m}{2\pi p} \left(-\frac{1}{2} (1 - e^{j\pi}) + e^{-j\pi} - 1 \right). \\
 e^{-j\pi p} &= e^{j\pi p} = (-1)^p, \text{ so } U_p^C = \frac{jU_m}{2\pi p} \left(-\frac{3}{2} + \frac{3}{2}(-1)^p \right) = \frac{j3U_m}{4\pi p} (-1 + (-1)^p). \\
 p=1 \quad U_1^C &= \frac{-j3U_m}{2\pi}, \quad U_1 = 2|U_1^C| = \frac{3}{\pi}U_m, \quad \rho_1 = \text{angle}(U_1^C) = -\frac{\pi}{2}. \\
 p=2 \quad U_2^C &= 0, \quad U_2 = 0. \\
 p=3 \quad U_3^C &= \frac{-jU_m}{2\pi}, \quad U_3 = 2|U_3^C| = \frac{1}{\pi}U_m, \quad \rho_3 = \text{angle}(U_3^C) = -\frac{\pi}{2}. \\
 \text{The three-order Fourier polynomial of } u_1(t) &\text{ is:} \\
 u_1(t) &\simeq U_m \left(0,25 + 0,9549 \cos\left(\frac{2\pi}{T}t - \frac{\pi}{2}\right) + 0,3183 \cos\left(\frac{6\pi}{T}t - \frac{\pi}{2}\right) \right). \\
 \text{b) } H(j\omega)|_{\omega=0} &= 0, \quad H(j\omega)|_{\omega=\frac{2\pi}{T}} = \frac{j2\pi}{2+j2\pi} = 0,9529e^{j0,3082} \\
 H(j\omega)|_{\omega=\frac{6\pi}{T}} &= \frac{j6\pi}{2+j6\pi} = 0,9944e^{j0,1057}. \\
 u_2(t) &= U_m \left[0,9099 \cos\left(\frac{2\pi}{T}t - 1,2626\right) + 0,3165 \cos\left(\frac{6\pi}{T}t - 1,4651\right) \right].
 \end{aligned}$$

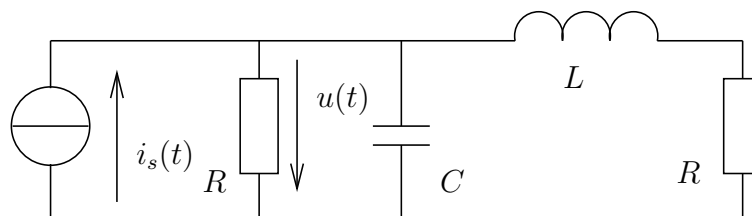2. The source current of the current source and the parameters of the network components are given: $i_s(t) = \left[20 + 10 \cos \omega_0 t + 5 \cos \left(2\omega_0 t - \frac{\pi}{6} \right) \right] \text{ mA}$, $\omega_0 = 2 \text{ krad/s}$, $R = 2 \text{ k}\Omega$, $L = 0,25 \text{ H}$, $C = 250 \text{ nF}$.



- Find the rms value of the source current!
- Find the time function of the noted $u(t)$ voltage!
- Find the average power of the current source!

Solution

a) $I_s = \sqrt{20^2 + \frac{10^2}{2} + \frac{5^2}{2}} \simeq 21,5058 \text{ mA}$.

- b) The suitable coherent unit system: $V, \text{ mA}, \text{ mW}, \text{ k}\Omega, \text{ H}, \text{ ms}, \mu\text{F}, \text{ krad/s}$.

At ω angular frequency the impedance of the two-pole connected to the source is:

$$Z(j\omega) = R \times \frac{1}{j\omega C} \times (R + j\omega L) = 2 \times \frac{1}{0,25j\omega} \times (2 + 0,5j\omega) = \frac{4+j\omega}{2+0,5j\omega+j\omega+0,25(j\omega)^2+2} =$$

$$= \frac{j\omega+4}{0,25(j\omega)^2+1,5j\omega+4} = \frac{4j\omega+16}{(j\omega)^2+6j\omega+16}, \quad Z(j\omega)|_{\omega=0} = 1,$$


$$Z(j\omega)|_{\omega=\omega_0=2} = \frac{16+j8}{12+j12} = 1,0541e^{-j0,3218}, \quad Z(j\omega)|_{\omega=2\omega_0=4} = \frac{16+j16}{j24} = 0,9428e^{-j\frac{\pi}{4}},$$

$$u(t) = [20 + 10,541 \cos(\omega_0 t - 0,3218) + 4,714 \cos(2\omega_0 t - 1,3090)]V.$$

$-18,43^\circ \qquad \qquad \qquad -75^\circ$

c) $P_s = (-20 \cdot 20 - \frac{1}{2} \cdot 10 \cdot 10,541 \cdot \cos(-0,3218) - \frac{1}{2} \cdot 5 \cdot 4,714 \cdot \cos(-1,309 + 0,5236)) \text{ mW} =$
 $= -458,33 \text{ mW}.$

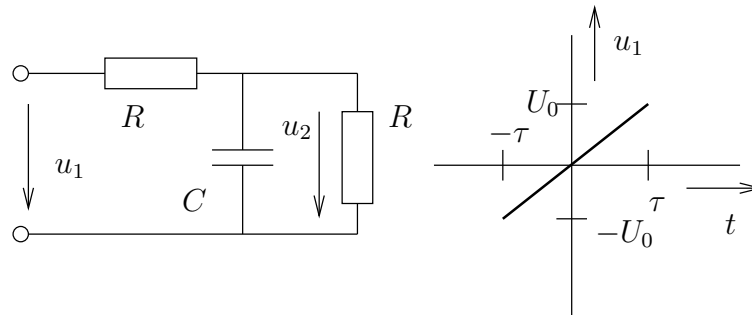3. The input signal and the response of the system represented by the given network are the u_1 and the u_2 voltages, respectively. The input signal is the voltage impulse drawn in the figure.



- Find the frequency response of the system represented by the network!
- Find the Fourier transform of the response signal!

Solution

a) $\bar{U}_2 = \bar{U}_1 \frac{R \times \frac{1}{j\omega C}}{R + R \times \frac{1}{j\omega C}}, \quad H(j\omega) = \frac{R \times \frac{1}{j\omega C}}{R + R \times \frac{1}{j\omega C}} = \frac{\frac{R}{1+j\omega CR}}{R + \frac{R}{1+j\omega CR}} = \frac{R}{R+j\omega CR^2+R} = \frac{\frac{1}{CR}}{j\omega + \frac{2}{CR}}.$

- b) We will find the spectrum of the input signal first.

$$U_1(j\omega) = \int_{-\infty}^{\infty} u_1(t) e^{-j\omega t} dt = \int_{-\tau}^{\tau} \frac{U_0}{\tau} t e^{-j\omega t} dt.$$

In the partial integration $(\int uv' = uv - \int u'v) \quad u = \frac{U_0}{\tau} t, \quad u' = \frac{U_0}{\tau}, \quad v' = e^{-j\omega t},$
 $v = \frac{1}{-j\omega} e^{-j\omega t}.$

$$U_1(j\omega) = \left[\frac{U_0}{\tau} t \frac{1}{-j\omega} e^{-j\omega t} \right]_{-\tau}^{\tau} - \frac{U_0}{-j\omega \tau} \int_{-\tau}^{\tau} e^{-j\omega t} dt = \frac{U_0}{-j\omega \tau} (\tau e^{-j\omega \tau} - (-\tau) e^{j\omega \tau}) -$$

$$- \frac{U_0}{(j\omega)^2 \tau} [e^{-j\omega t}]_{-\tau}^{\tau} = \frac{j2U_0}{\omega} \cos \omega \tau + \frac{U_0}{\omega^2 \tau} (e^{-j\omega \tau} - e^{j\omega \tau}) = \frac{j2U_0}{\omega} \cos \omega \tau + \frac{U_0}{\omega^2 \tau} (-2j \sin \omega \tau) =$$

$$= j \frac{2U_0}{\omega} \left(\cos \omega \tau - \frac{\sin \omega \tau}{\omega \tau} \right).$$

The Fourier transform of the response signal is: $U_2(j\omega) = j \frac{2U_0}{\omega} \left(\cos \omega \tau - \frac{\sin \omega \tau}{\omega \tau} \right) \frac{\frac{1}{CR}}{j\omega + \frac{2}{CR}}.$