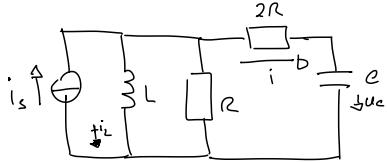





Signals and Systems 2

2023. 9. 10 Trauma



what's the transfer characteristic?

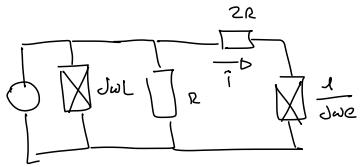

$$H(j\omega) = \frac{R \times j\omega L}{R \times j\omega L + 2R + \frac{1}{j\omega C}}$$

$$\frac{\frac{(R + j\omega L)}{R + j\omega L}}{\frac{R \cdot j\omega L}{R + j\omega L} + \frac{2R\omega + 2R}{j\omega C}} = \frac{R j\omega L}{R j\omega L + 2R^2 + \frac{R}{j\omega C} + 2R j\omega L + \frac{j\omega L}{j\omega C}}$$

$$\frac{(j\omega)^2 RLC}{3(j\omega)^2 R C + 2\omega^2 j\omega C + j\omega L} = \frac{\frac{1}{3}(j\omega L)^2}{(j\omega)^2 + j\omega \left(\frac{2\omega}{3C} + \frac{1}{3RC}\right)} + \frac{1}{3LC}$$

HW: check SVD

$$\dot{u}_c = ?$$

$$\varphi = L \dot{i}_L$$

$$\dot{i}_L = ?$$

$$i = ? \cdot (C \dot{u}_c)$$

$$H(j\omega) = \frac{3j\omega + 6}{(\omega)^2 + 4j\omega + 9}$$

$$y(t) = \underbrace{\text{c.u.o.s}}_{RL} + \underbrace{\text{osc}}_L$$

$$L = 0.4 \quad R = 5 \Omega$$

$$\underline{S} = ?$$

$$w \quad \bar{u} \quad \bar{H}$$

$$0 \quad -10 \quad \frac{6}{5}$$

$$+ 3 \cdot \cos(5t - 70^\circ)$$

$$+ 4e^{j15^\circ} \quad \frac{3}{4}$$

$$5 \quad 3e^{-j40^\circ} \quad 0.6307e^{-j60^\circ}$$

$$H(s) = \frac{3s+6}{s^2 + 4s + 9}$$

$$H(s) = \frac{15s + 6}{s^2 + 20s + 25}$$

$$= 3e^{j15^\circ} \cdot 1.89e^{-j70.5^\circ}$$

$$y(t) = \left[\frac{60}{9} + 3 \cos(t + 15^\circ) + 4.89 \cos(5t - 70.5^\circ) \right] \text{mA}$$

$$\underline{Z}_o =$$

$$\underline{S}_o = (i)^2 \underline{Z} = i^2 \cdot R = \left(\frac{60}{9} \right)^2 \cdot 5 = \frac{2000}{9}$$


$$\underline{S}_r = \frac{1}{2} (i)^2 \underline{Z} = \frac{1}{2} (3)^2 \cdot (3 + j0.4) = \frac{9\sqrt{62.9}}{10} e^{j4.57^\circ}$$

$$\underline{S} = \frac{1}{2} (i)^2 \underline{Z} = \frac{1}{2} (1.89)^2 \cdot (3 + j0.4 \cdot 5) = 9.648 e^{j24.8^\circ}$$


$$\underline{S} = \frac{2000}{9} + \frac{9\sqrt{62.9}}{10} \cos(t + 4.57^\circ) + 9.648 \cos(5t + 24.8^\circ)$$

$$I_{RMS} = \sqrt{\left(\frac{60}{9} \right)^2 + \frac{3^2 + 1.89^2}{2}}$$

$$I_{RMS}^2 \cdot S = A + B + D$$

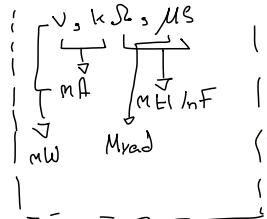

2025. 9. 10
Example 1
RE DD
at home

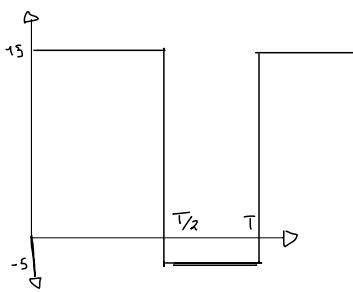

2025. 9. 10

Example 2

re do at home

$$\sqrt{\frac{1}{T} \int_0^T (u(t))^2 dt} = \sqrt{\frac{1}{T} \left[\int_0^{T/2} 15^2 dt + \int_{T/2}^T (-5)^2 dt \right]} = \sqrt{\frac{1}{T} \cdot 125T} = \sqrt{125} = 11.18$$

$$u_0 = \frac{1}{T} \int_0^T u(t) dt = \frac{1}{T} \left[\int_0^{T/2} 15 dt + \int_{T/2}^T -5 dt \right] = 5$$

$$\bar{u}_1 = \frac{1}{T} \left[\int_0^{T/2} 15 e^{-j\omega_0 t} dt + \int_{T/2}^T -5 e^{-j\omega_0 t} dt \right]$$

$$= \frac{1}{T} \left(\frac{15}{-\omega_0} \left[e^{-j\omega_0 \frac{T}{2}} - 1 \right] + \frac{5}{\omega_0} \left[e^{-j\omega_0 T} - e^{-j\omega_0 \frac{T}{2}} \right] \right)$$

$$= \frac{1}{\pi j 2\omega_0} \left(15 \left(1 - e^{-j\frac{\pi}{2}} \right) + 5 \left(e^{j\frac{3\pi}{2}} - e^{-j\frac{3\pi}{2}} \right) \right)$$

$$= \frac{1}{\pi j 2\omega_0} (20 - 20 e^{-j\pi})$$

$$\bar{u}_1 = \frac{1}{\pi j 2\omega_0} (20 + 20) = \frac{20}{\pi j \omega_0}$$


$$\bar{u}_2 = \frac{1}{\pi j 4\omega_0} (20 - 20) = \phi$$


$$\bar{u}_3 = \frac{1}{\pi j 6\omega_0} (20 + 20) = \frac{20}{3\pi j \omega_0}$$

$$u(t) = 5 + \frac{40}{\pi} \cos(\omega_0 t - \frac{\pi}{2}) + 0 + \frac{40}{3\pi} \cos(3\omega_0 t - \frac{\pi}{2})$$

Third order approx of fourier series

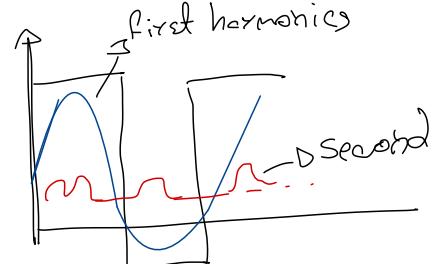
$$u_{RMS} = \sqrt{3^2 + \frac{\left(\frac{40}{\pi}\right)^2 + \left(\frac{40}{3\pi}\right)^2}{2}} = 11.535$$



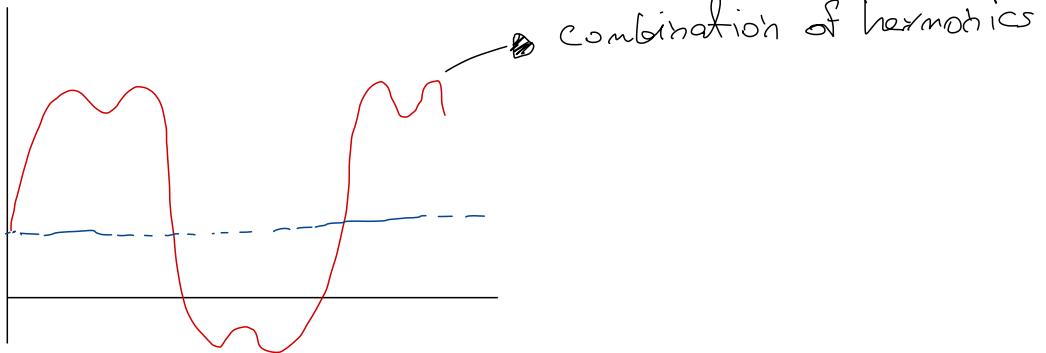

combination of harmonics

Example 3 2023. 9. 10

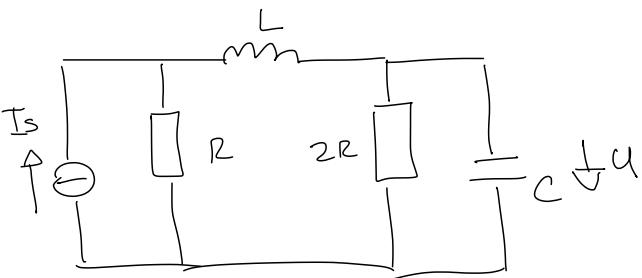

$$H(j\omega) = \frac{I}{U} \cdot \frac{\frac{R}{j\omega C}}{\frac{1}{j\omega C} + 2R + j\omega L + R} \cdot \frac{\frac{2R}{j\omega C}}{2R + \frac{1}{j\omega C}} \cdot \frac{\frac{1}{j\omega C}}{j\omega C}$$

$$H(j\omega) = \frac{\frac{R}{j\omega C} \cdot 2R}{\frac{1}{j\omega C} + 2R} + j\omega L + R \cdot \frac{2R}{\left(2R + \frac{1}{j\omega C}\right) \frac{1}{j\omega C}} =$$

$$\frac{\frac{2R^2}{j\omega C}}{\frac{2R}{j\omega C} + 2Rj\omega L + 2R^2 + \frac{j\omega L}{j\omega C} + \frac{R}{j\omega C}} =$$


$$\frac{\frac{2R^2}{j\omega C}}{2R + 2R(j\omega)^2 LC + 2R^2(j\omega C) + j\omega L + \frac{R}{j\omega C}} =$$

$$= \left(\frac{\frac{2R^2}{j\omega C}}{3R + j\omega L + (j\omega)^2 2R LC + 2R^2 j\omega C} \right) = \begin{bmatrix} \frac{R}{LC} \\ \left(j\omega \right)^2 + j\omega \left(\frac{1}{2RC} + \frac{R}{L} \right) + \frac{3}{2LC} \end{bmatrix}$$

correct transfer charact
ristic

$$H(j\omega) = \left[\frac{R}{LC} + (j\omega)^2 + j\omega \left(\frac{1}{2RC} + \frac{R}{L} \right) + \frac{3}{2LC} \right]^{-1}$$

$U_{ct} = ?$

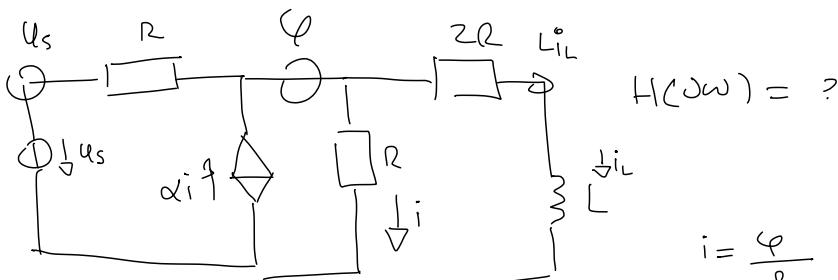

$$H(j\omega) = ?$$

$$\varphi: \frac{\varphi - U_s}{R} + \frac{\varphi}{R} + \frac{\varphi - L^o_i}{2R} - \alpha i = \emptyset$$

$$2\varphi - 2U_s + 2\varphi + \varphi - L^o_i - 2R\alpha i$$

$$5Ri - 2U_s - L^o_i - 2R\alpha i = \emptyset$$

$$\frac{L^o_i - Ri}{2R} + i_L = \emptyset$$

$$5R \left(\frac{L^o_i + 2i_L}{R} \right) - 2U_s - L^o_i - 2R\alpha \left(\frac{L^o_i + 2i_L}{R} \right)$$

$$L^o_i = Ri - 2Ri_L$$

$$i = \frac{L^o_i + 2i_L}{R}$$

$$= 5L^o_i + 10Ri_L - 2U_s - L^o_i$$

$$- \frac{2\alpha L^o_i}{R} - 4R\alpha i_L = \emptyset$$

$$i_L (10R - 4R\alpha)$$

$$= 4L^o_i - 2\alpha L^o_i - 2U_s + 4Ri_L - 4R\alpha i_L =$$

$$L^o_i (4 - 2\alpha) = i_L (4R\alpha - 10R) + 2U_s$$


$$i_L = \frac{i_L (4R\alpha - 10R) + 2U_s}{(4 - 2\alpha)L} + \frac{2U_s}{(4 - 2\alpha)L}$$

$$H(j\omega) = C^T (j\omega I - A)^{-1} B + D$$

$$\frac{-1}{2 - \alpha} \quad \frac{1}{j\omega + \frac{5\alpha \times R}{\alpha - \alpha_1 L}} \quad \frac{1}{(2 - \alpha)L} + \frac{1}{(2 - \alpha)R}$$

2025.9.15

Fourier Transform

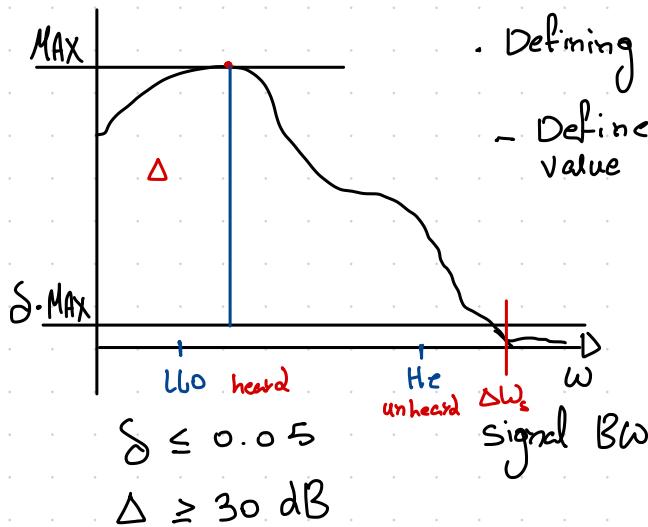


- Defining signal bandwidth
 - Define some % of max value

Network vs Signal BW

How do we determine network BW?

$$k(\omega) = |H(j\omega)|$$


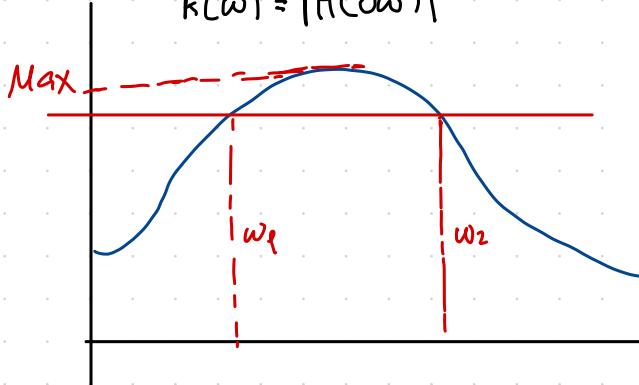


$$\begin{aligned} \delta &\geq 0.7 \\ \Delta &\leq 30 \text{ dB} \\ \text{limit: } &\frac{1}{\sqrt{1 + \varepsilon^2}} \quad \varepsilon \leq 1 \end{aligned}$$

All pass system


- All frequencies transferred through the network.

low p. system

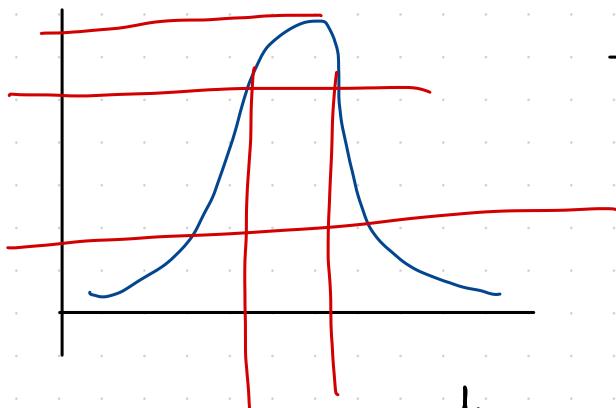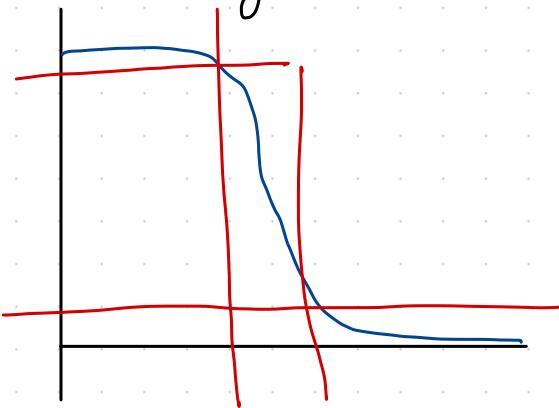


B p.

radios

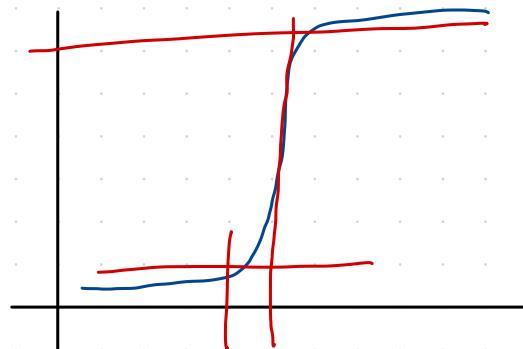

H pass

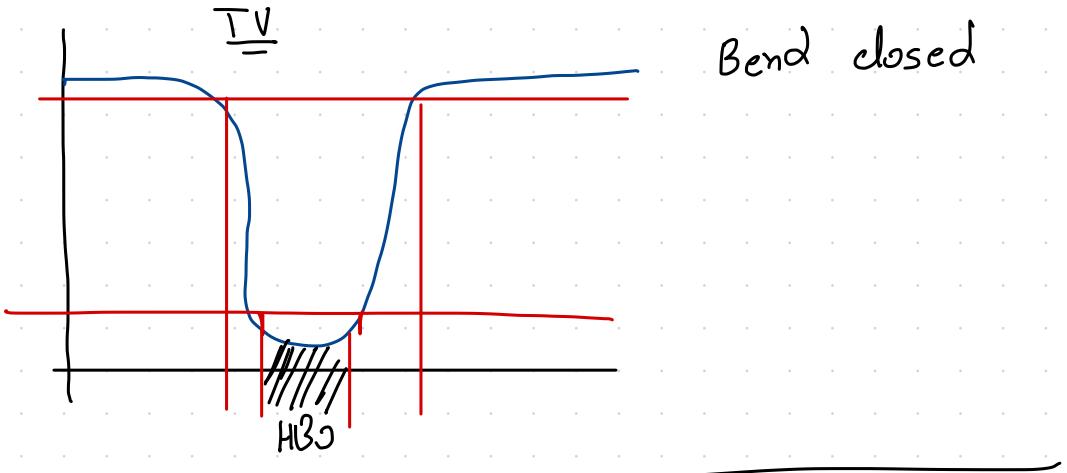

$$u_s(t) = 10 \cdot e^{-4t} \varepsilon(t)$$

BW of Signal ?

Suppose signal Spectrum

$$\delta = 0.02$$

1. Determine spectrum

$$F\left\{ u_s(t) \right\} = \int_{-\infty}^{\infty} u_s(t) e^{-j\omega t} dt = \int_{0}^{\infty} 10 e^{-4t} e^{-j\omega t} dt =$$

$$\frac{10 (e^{-4\omega} - e^{-4 \cdot 0 j\omega})}{-4 - j\omega} = \frac{10}{j\omega + 4}$$

$$\left| \frac{10}{j\omega + 4} \right| = \frac{10}{\sqrt{\omega^2 + 4^2}} \Bigg|_{\omega=0} = \frac{10}{4} \text{ Max Value}$$

$f(t)$	$\mathcal{F}(j\omega)$
$\delta(t)$	1
$\mathcal{E}(t)$	$\frac{1}{j\omega} + \pi S(j\omega)$
$\mathcal{E}(t) \cdot e^{-\alpha t}$ $ \alpha > 0$	$\frac{1}{j\omega + \alpha}$
$t \cdot \mathcal{E}(t) e^{-\alpha t}$	$\frac{1}{(j\omega + \alpha)^2}$
$e^{-\alpha t }$	$\frac{2 \alpha}{\alpha^2 + \omega^2}$

if u have an even function the fourier of the system will always be a real function

2. everything below 0.02 is neglected

$$S_{\text{Max}} = \frac{10}{\sqrt{\omega_s^2 + 4^2}} = 0.02 \cdot \frac{10}{4} = \frac{10}{\sqrt{\omega_s^2 + 4^2}}$$

$$\sqrt{\omega_s^2 + 4^2} = \frac{4}{0.02} = 200$$


$$\omega_s^2 = 40000 - 16 = 39984$$

$$\omega_s = \sqrt{39984} = 199.96$$

199 or 200

which?


200

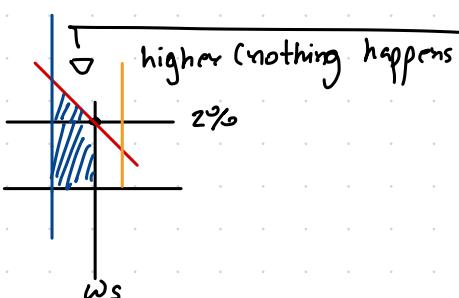

$\mathcal{E}(t)$ has no fourier transform because it is not absolute integrable


$$\left(\frac{1}{\alpha - j\omega} \right)$$

$$e^{-\alpha |t|} = \mathcal{E}(-t) \cdot e^{-\alpha t} + \mathcal{E}(t) e^{-\alpha t}$$

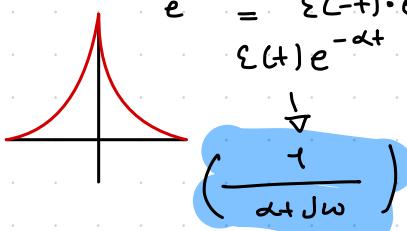

$$\frac{\alpha + j\omega + \alpha - j\omega}{\alpha^2 + \omega^2} = \frac{2\alpha}{\alpha^2 + \omega^2}$$

3. Transfer system to a complicated one

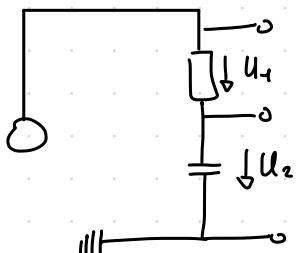

$$R = 2 \Omega$$

$$\Delta = 1 \text{ dB}$$

$$C = ?$$

$$H_1(j\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{j\omega RC + 1} =$$

Bode diagram

high pass system

$$H_2(j\omega) = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{Rj\omega C + 1} =$$

$$= \frac{1/RC}{j\omega + 1/RC}$$

low pass system

$$| k |_{\max} = ? = \frac{1/RC}{\sqrt{\omega^2 + (1/RC)^2}} \Big|_{\omega=1}$$

$$L_D = -10 \log(?) \quad (20 \log(1)) \downarrow \quad \downarrow \quad 10^{-\frac{1}{20}}$$

How to calculate $\Delta = 1$?

$$= 0.89$$

$$\frac{-1}{-1 \text{ dB}} \rightarrow \text{Amp} \Rightarrow \frac{-1}{10 \frac{1}{20}} = 0.89$$

$$0.89 = \frac{1}{\sqrt{(200)^2 + (\frac{1}{2C})^2}}$$



$$(0.89) \sqrt{(200)^2 + (\frac{1}{2C})^2}$$

$$C = ?$$

$$L_D 17, 26$$



$$S_M + \frac{1}{\alpha}$$

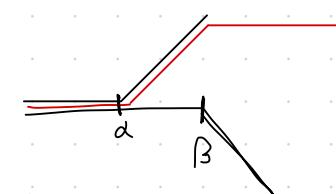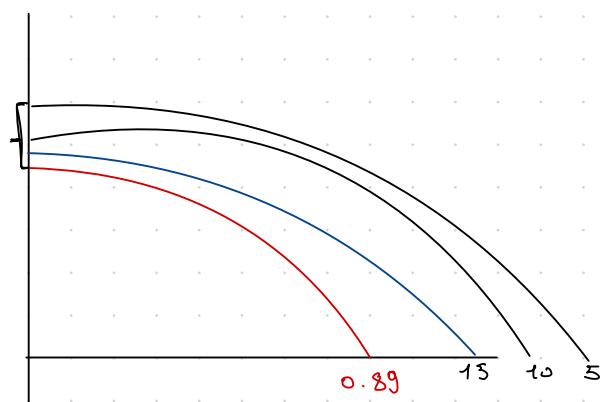

if $\frac{d}{B} > 1$, LP V
if $1 > \frac{d}{B}$, HP A
 $\omega = \emptyset$

$$\frac{j\omega + d}{j\omega + B}$$


Third approx

$$H(j\omega) = \frac{j\omega^2 + 4j\omega}{(j\omega + 2)(j\omega + 8)}$$

$$(1 + j \frac{\omega}{\omega_0})$$

$$\frac{j\omega(\frac{j\omega+1}{4}) \cdot 4}{(1 + j \frac{\omega}{2})(4 + j \frac{\omega}{8})} \cdot 16$$


$\log(0.25)$

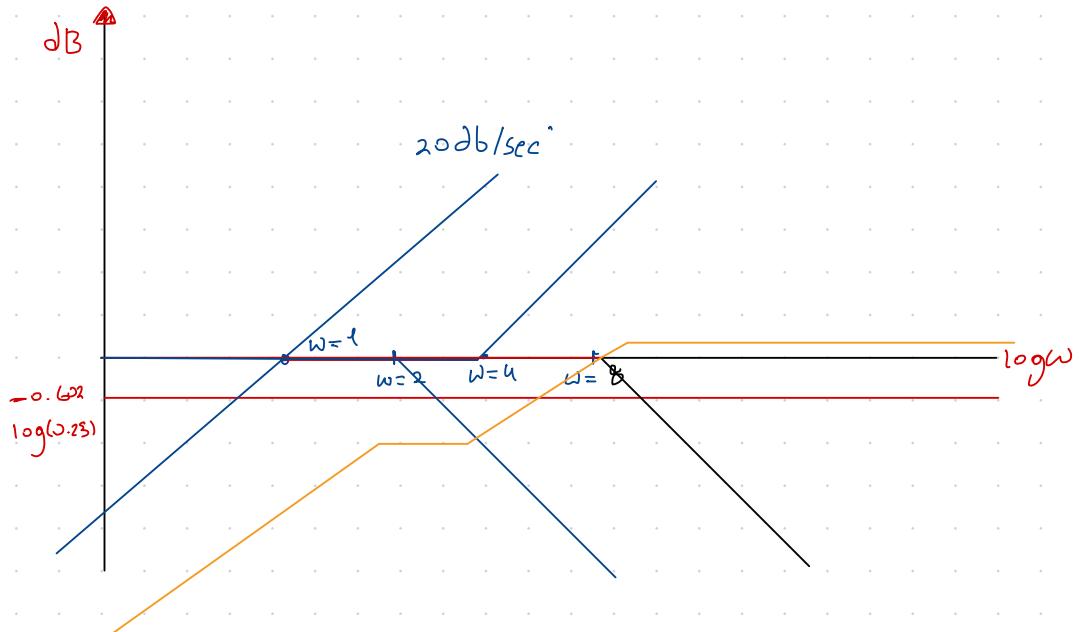

2025. 9. 17

Fourier transform Examples

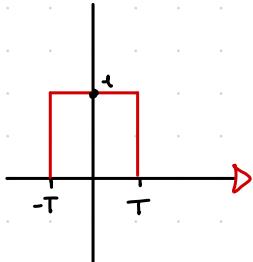
$\cdot \mathcal{E}(t)$ is not integrable, $\mathcal{E}(t) \rightarrow \frac{1}{j\omega} + \pi \delta(t)$




$$\int_{-T}^T e^{-j\omega t} dt = \frac{e^{-j\omega T} - e^{j\omega T}}{-j\omega} = \frac{e^{j\omega T} - e^{-j\omega T}}{2j\omega T}$$

$$= 2T \frac{2 \sin \omega T}{\omega T}$$
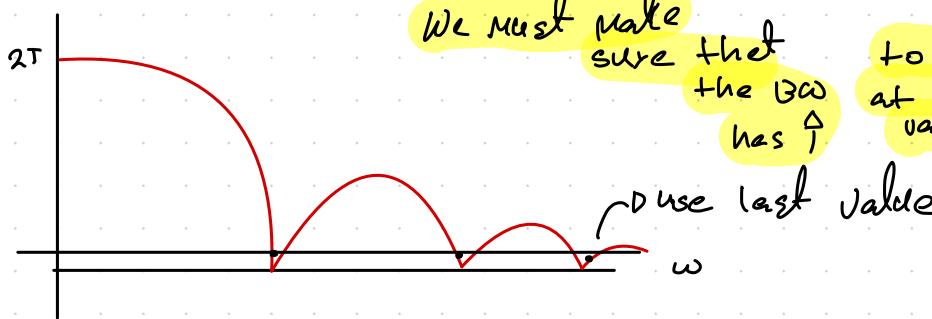
$$\frac{1}{j\omega} e^{j\omega T} - \frac{1}{j\omega} e^{-j\omega T}$$



Shift using shifting theorem

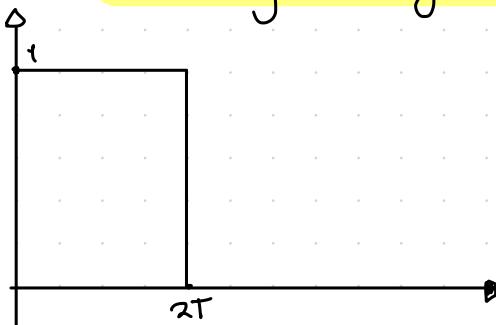


$$\mathcal{F} \left\{ x(t-T) \right\} = X(j\omega) e^{-j\omega t}$$


$$2T \cdot \frac{\sin(\omega T)}{\omega T} \cdot e^{-j\omega t}$$

$$\int_0^{2T} e^{-j\omega t} \cdot dt = \frac{e^{-2j\omega t} - 1}{-j\omega}$$
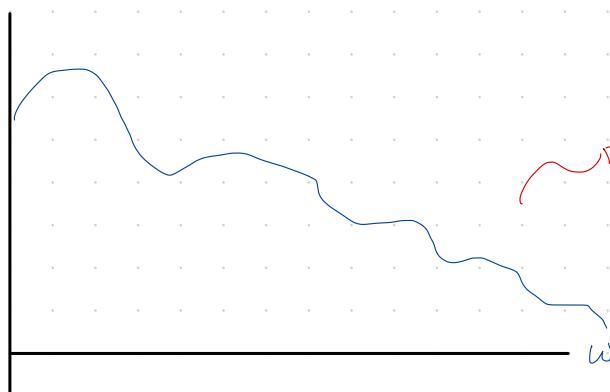
$$= \frac{1}{j\omega} - \frac{e^{-2j\omega t}}{j\omega} =$$




Non periodic
Function

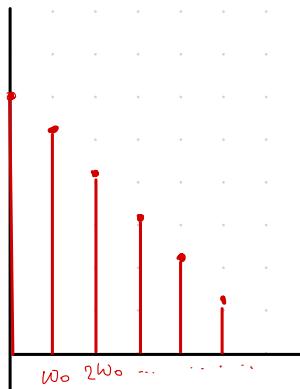

Periodic

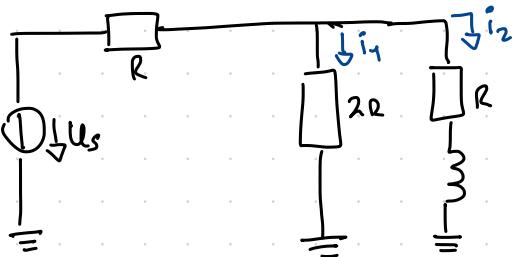use to determine
if we need a HPass/
LPass



$$R = 5$$

$$L = 0.4$$

$$\Delta_N = 1 \text{ dB}$$

$$U_s(t) = 10e^{-\alpha t} e^{j\omega t}$$

$$\delta = 0.01$$

$$\omega = 0 \frac{1}{\sqrt{5R}}$$

$$\omega = \infty \frac{1}{\sqrt{3R}}$$

$$H_1(j\omega) = \frac{2R \times (R + j\omega L)}{R + 2R \times (R + j\omega L)} \cdot \frac{1}{2R} = \frac{2R + 2j\omega L}{3R + 3j\omega L} \cdot \frac{1}{2R} = \frac{2R + 2j\omega L}{2R(5R + 3j\omega L)}$$

$\sqrt{\frac{1}{5R}}$

$$H_2(j\omega) = \frac{2R \times (R + j\omega L)}{R + 2R \times (R + j\omega L)} \cdot \frac{1}{R + j\omega L} = \frac{2R + 2j\omega L}{3R + 3j\omega L} \cdot \frac{1}{R + j\omega L} = \frac{\frac{2}{3R}}{\frac{3\omega + \frac{5R}{3}}{3R}}$$

$$\text{Bode } \omega = 0, \frac{L}{3R}$$

Why we need a low B_p ?

$$\frac{10}{j\omega + \alpha} \text{ Max } \left|_{\omega=0} \right. = \frac{10}{\alpha}$$

$$\frac{10}{\sqrt{\omega^2 + \alpha^2}}$$

$2 / 2.5 / 3$

use to determine

$$0.01 \cdot \frac{10}{\alpha} \leq \frac{10}{\sqrt{\omega_H + \alpha^2}}$$

use to find α

Suppose

$\alpha = 2$? ω_2 is the answer in this case

$\alpha = 2.5$

3 ?

$$u_s(t) = 4 \cdot e^{2t+1}$$

$$A = \begin{vmatrix} -2 & 1 \\ -3 & -4 \end{vmatrix}$$

$$k(\omega) = \frac{\frac{2}{3L}}{\sqrt{\omega^2 + \left(\frac{8R}{3L}\right)^2}}$$

$$\text{Max} = \frac{2}{2S}$$

$$10 \cdot \frac{\frac{1}{20}}{\sqrt{\omega_0^2 + \left(\frac{2S}{4.2}\right)^2}}$$

$$\omega_0 = \sqrt{\left(\frac{\frac{2}{4.2}}{10 \cdot \frac{1}{20} \cdot \frac{2}{2S}}\right)^2 - \left(\frac{2S}{4.2}\right)^2}$$

$$= 23.28$$

ω_0 ↗

2023.9.17

2025. 9. 17

Laplace Transform vs Fourier Transform

↓
Mathematical equation

• LDT time domain



complex domain

$$G + j\omega \rightarrow S$$

$$\tilde{F}(s) = \int_{-\infty}^{\infty} f(t) e^{-st} dt$$

bc

$$\Delta t \rightarrow -\phi \rightarrow +\phi$$

• function can be
any kind of function

• doesn't have to be
integrable

↓
Signal time domain
Spectrum
↓
Signal domain

$$\text{rep: } \int f(t) e^{-j\omega t} dt$$



$$\frac{1}{2\pi} \int_{-\infty}^{\infty} \tilde{f}(\omega) e^{j\omega t} d\omega$$

• professor hasn't used
his entire life


$$G + j\omega$$

$$\frac{1}{2\pi j} \int_{G-j\infty}^{G+j\infty} \tilde{F}(s) e^{st} ds$$

Riemann Mellin

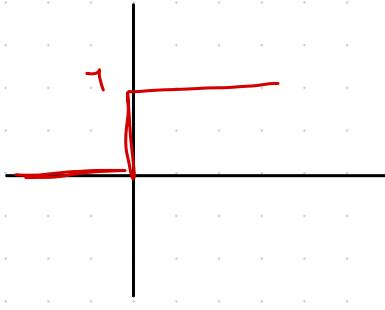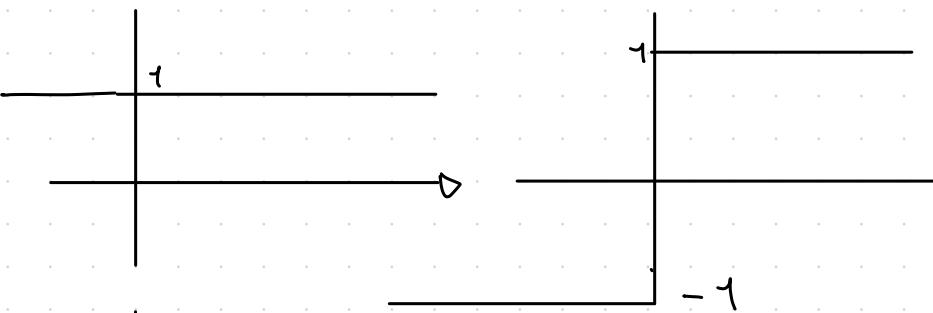

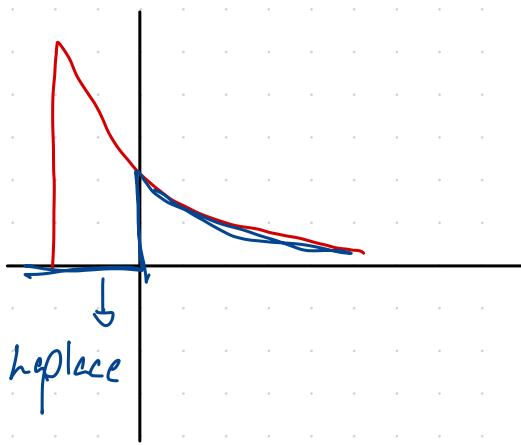- if function is causal we can't recover it
- all functions have an Laplace transform
- cuts everything before ϕ



$f(t)$	$F(s)$
$s \epsilon(t)$	1
$\epsilon(t)$	$\frac{1}{s}$
$t \epsilon(t)$	$1/s^2$
$t^n \epsilon(t)$	$n! / s^{n+1}$
$\epsilon(t) e^{-at}$	$1/(s+a)$
$\epsilon(t) \cos \omega_0 t$	$\frac{s}{s^2 + \omega_0^2}$
$\epsilon(t) \sin \omega_0 t$	$\frac{\omega_0}{s^2 + \omega_0^2}$
$\epsilon(t-T) \epsilon(t-T)$	$\epsilon(s) \cdot e^{-st}$

W2H3 9.18

• Laplace transform.

$$\text{I. } \mathcal{L} \{ x(t) + y(t) \} = \mathcal{L} \{ c x(t) \} + \mathcal{L} \{ c y(t) \}$$

$$\text{II. } \mathcal{L} \{ x(t) \cdot e^{-\alpha t} \} = x(s + \alpha) \quad \int_{-\infty}^{\infty} x(t) \cdot e^{-st} dt$$

$$\text{III. } \mathcal{L} \{ x(t) \cdot e^{-j\omega_0 t} \} = X(s + j\omega_0) \quad \int_{-\infty}^{\infty} x(t) \cdot e^{-st} dt = \frac{e^{-s\omega_0} - e^{-s\infty}}{-s} = \frac{1}{s}$$

$$\text{IV. } \mathcal{L} \{ \dot{x}(t) \} = s \cdot \mathcal{L} \{ x(s) \} + x(-\phi) \quad x(t) \cdot \cos \omega_0 t = \frac{x(t) \cdot e^{j\omega_0 t} + e^{-j\omega_0 t}}{2}$$

$$\text{V. } \mathcal{L} \left\{ \int_0^{\infty} x(t) dt \right\} = \frac{x(s)}{s} \quad \frac{1}{2} \left(\frac{1}{s - j\omega_0} + \frac{1}{s + j\omega_0} \right) = \frac{s}{s^2 + \omega_0^2}$$

$$\text{VI. } x(t = \pm 0) = \lim_{s \rightarrow \infty} s \mathcal{L} \{ x(s) \}$$

$$\text{VII. } x(t \rightarrow \infty) = \lim_{s \rightarrow 0} s \mathcal{L} \{ x(s) \}$$

$$\text{VIII. } \mathcal{L} \{ \int_0^t x(t-T) x(t-T) dt \} = x(s) e^{-sT}$$

$$\text{IX. } \mathcal{L} \{ h(t) * u(t) \} = \mathcal{L} \{ h(t) \} \cdot \mathcal{L} \{ u(t) \}$$

t	R	L	C		in complex domain	Rewrite Notes
$j\omega$	R	$j\omega L$	$\frac{1}{j\omega C}$	CD	frequency is not changed	at home
s	R	SL	$\frac{1}{sC}$	LD	eddy currents on wires shift resistivity a bit	

$$u_L = L \cdot \frac{di}{dt} \quad i_c = C \dot{u}_c$$

$$U_L(s) = L \cdot s I(s)$$

$\bullet a(t) = \mathcal{E}(t)(3e^{-4t} + 6e^{-7t}) \Rightarrow \frac{3}{s+4} + \frac{6}{s+7} \cancel{\times} \frac{9s+48}{s^2 + 11s + 28}$

$\int_0^\infty 3e^{-4t} \cdot e^{-st} dt = 3 \int_0^\infty e^{-(s+4)t} dt$

write this way

$$(s+4) \cdot (s+7)$$

$\bullet b(t) = \mathcal{E}(t) \cdot 3 \cdot t \cdot e^{-4t}$ (use table)

What's the Laplace?

$$B(s) = \frac{3}{(s+4)^2}$$



$\bullet c(t) = [\mathcal{E}(t) - \mathcal{E}(t-T)] 3 \cdot e^{-4t} = 3e^{-4t} \mathcal{E}(t) - \mathcal{E}(t-T) 3e^{-4t}$

$$\begin{aligned} & 3e^{-4t} \mathcal{E}(t) - \mathcal{E}(t-T) 3e^{-4(t-T)} \\ &= \mathcal{E}(t) 3e^{-4t} - \mathcal{E}(t-T) 3e^{-4(t-T)} \\ &= \frac{3}{s+4} - \frac{3e^{-4T}}{s+4} e^{-sT} \end{aligned}$$

$$\frac{1}{s+4} (3 - 3e^{-4T} e^{-sT})$$

implies

Rewrite Notes on new abc !!!


function will be shifted.

$$d(t) = [\varepsilon(t) - \varepsilon(t-T)] 3 + e^{-4t} = 3 + e^{-4t} \varepsilon(t) - \varepsilon(t-T) 3 + e^{-4t}$$

$$= \varepsilon(t) 3 + e^{-4t} - \varepsilon(t-T) 3(t-T+T) e^{-4(t-T)} =$$

$$\varepsilon(t) 3 + e^{-4t} - \varepsilon(t-T) 3(t-T+T) e^{-4(t-T)} \varepsilon(t-T) 3 + e^{-4(t-T)}$$
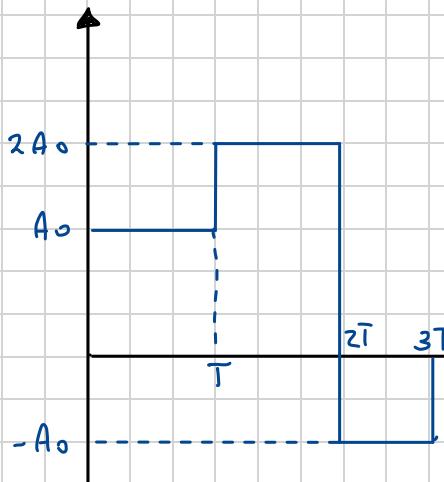
$$3/(s+4)^2 - \frac{3e^{-4T} \cdot e^{-sT}}{(s+4)^2} - \frac{3Te^{-4T}}{s+4} e^{-sT}$$



$$e(t) = A_0 \varepsilon(t) + A_0 \dot{\varepsilon}(t-T) - 3A_0 \varepsilon(t-2T) + A_0 \varepsilon(t-3T)$$


$$e(t) = [\varepsilon(t) - \varepsilon(t-T)] A_0 +$$


$$[\varepsilon(t-T) - \varepsilon(t-2T)] 2A_0 + [\varepsilon(t-2T) - \varepsilon(t-3T)] (-A_0)$$

$$E(s) = \frac{1}{s} (A_0 + A_0 e^{-sT} - 3A_0 e^{-s2T} + A_0 e^{-s3T})$$


$$[\varepsilon(t) - \varepsilon(t-T)] \frac{6A_0}{T} + [\varepsilon(t-T) - \varepsilon(t-2T)] 2A_0$$

remaining is in gallery

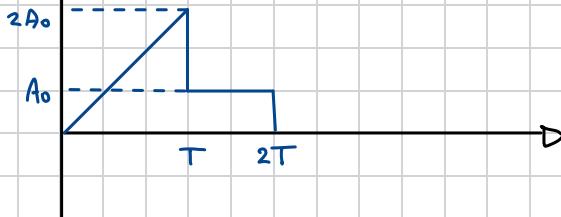


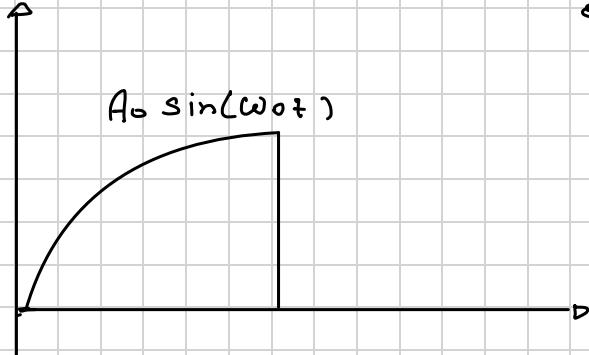

on gallery

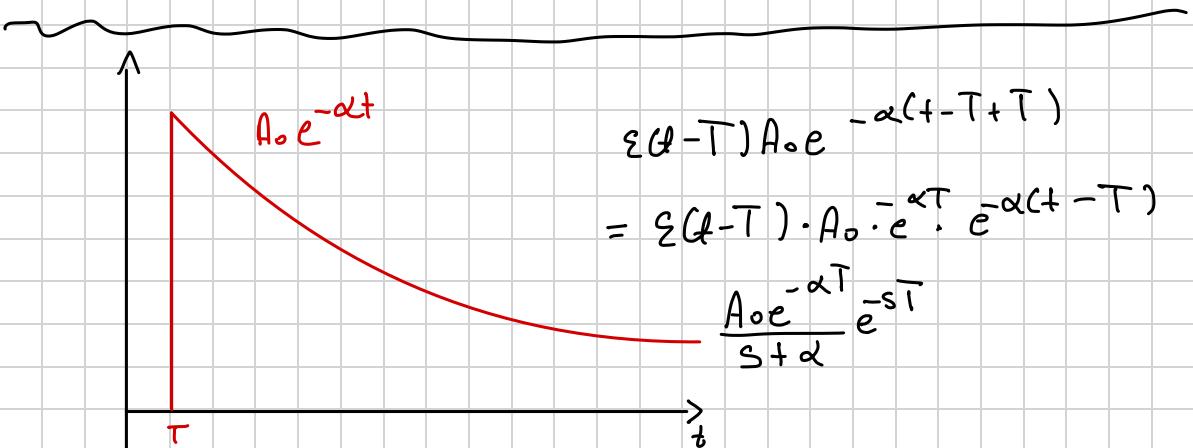
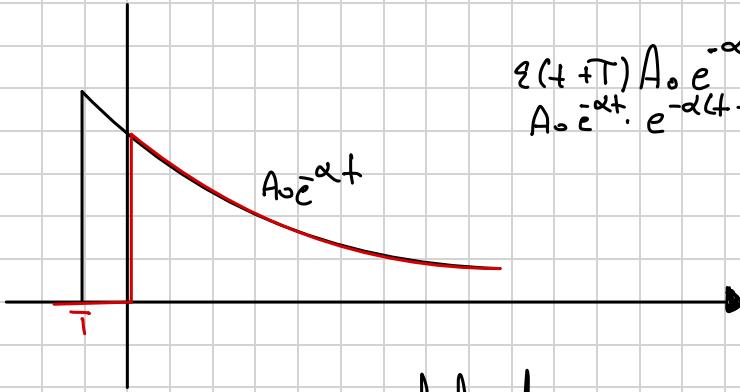
$$\begin{aligned}
 \mathcal{E}(t+T) A_0 e^{-\alpha(t-T+T)} &= \mathcal{E}(t+T) \cdot \\
 A_0 e^{-\alpha t} \cdot e^{-\alpha(t+T)} &= \frac{A_0 e^{\alpha T}}{s+\alpha}
 \end{aligned}$$



Non real fraction polynomial division

$$\begin{aligned}
 F(s) &= \frac{3s^2 + 4s + 6}{s^2 + 8s + 12} = \frac{3s^2 + 4s + 6}{(s+6)(s+2)} = 3 - \frac{20s - 30}{(s+6)(s+2)} \\
 &\quad \left. \begin{array}{r} \\ -3s^2 - 24s - 36 \\ \hline -20s - 30 \\ -20s - 160 - \frac{240}{s} \\ \hline 130 + \frac{240}{s} \end{array} \right\} \frac{1}{3} \\
 &\quad \left. \begin{array}{r} \\ 3s^2 + 24s + 36 \\ \hline -20s - 30 \\ -20s - 160 - \frac{240}{s} \\ \hline 130 + \frac{240}{s} \end{array} \right\} \frac{1}{3} \\
 &\quad \left. \begin{array}{r} \\ 3s^2 + 4s + 6 \\ \hline -20s - 30 \\ (s+6)(s+2) \end{array} \right\} 3 - \frac{20}{s} + \frac{130}{s^2} \\
 &\quad \left. \begin{array}{r} \\ 3s^2 + 4s + 6 \\ \hline -20s - 30 \\ (s+6)(s+2) \end{array} \right\} 3s(s) - 20s(s) + \\
 &\quad \left. \begin{array}{r} \\ 3s^2 + 4s + 6 \\ \hline -20s - 30 \\ (s+6)(s+2) \end{array} \right\} 130 + \frac{240}{s} + \dots
 \end{aligned}$$

$$A(s+2) + B(s+6) = -20s - 30$$

$$A + B = -20 \quad A = \frac{-90}{4}$$

$$2A + 6B = -30$$

$$B = \frac{10}{4}$$

